

浙江大学

本科实验报告

课程名称: 计算机逻辑设计基础

姓 名: 仇国智

学 院: 竺可桢学院

专 业: 计算机科学与技术

学 号: 3220102181

指导教师: 董亚波

2023 年 11 月 10 日

一、实验目的和要求

1 实验目的

- 1.1 掌握典型同步时序电路的工作原理和设计方法
- 1.2 掌握时序电路的激励函数、状态图、状态方程的运用
- 1.3 掌握用 Verilog 进行有限状态机的设计、调试、仿真
- 1.4 掌握用 FPGA 实现时序电路功能

2 实验任务

- 2.1 任务 1：原理图方式设计 4 位同步二进制计数器
- 2.2 任务 2：以 Verilog 行为描述方式设计 16 位可逆二进制同步计数器

二、实验内容和原理

1 实验内容

- 1.1 任务 1：原理图方式设计 4 位同步二进制计数器
- 1.2 任务 2：以 Verilog 行为描述方式设计 16 位可逆二进制同步计数器

2 实验原理

- 2.1 构 4 位二进制同步计数器：根据 D 触发器原理，在 clk 作用下 $Q = D$ ，4 位计数器的 Q 和 D 关系如下表

	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
10	0	1	0	1	1	1	0	1
11	1	1	0	1	0	0	1	1
12	0	0	1	1	1	0	1	1
13	1	0	1	1	0	1	1	1
14	0	1	1	1	1	1	1	1
15	1	1	1	1	0	0	0	0

根据真值表化简得表达式：

$$\begin{aligned}D_A &= \overline{Q_A} \\D_B &= \overline{Q_A}Q_B + Q_A\overline{Q_B} = \overline{Q_A} \oplus \overline{Q_B} \\D_C &= \overline{Q_A}Q_C + \overline{Q_B}Q_C + Q_AQ_B\overline{Q_C} \\&= (\overline{Q_A} + \overline{Q_B}) \oplus \overline{Q_C} \\D_D &= \overline{Q_A}Q_D + \overline{Q_B}Q_D + \overline{Q_C}Q_D + Q_AQ_BQ_C\overline{Q_D} \\&= (\overline{Q_A} + \overline{Q_B} + \overline{Q_C}) \oplus \overline{Q_D}\end{aligned}$$

2.2 可逆二进制同步计数器：可逆二进制同步计数器通过控制端 S 选择正向或者反向计数。S=1 时，正向计数。S=0 时，反向计数。各触发器逻辑表达式如下式：

$$\begin{aligned}
 D_A &= \overline{Q_A} \\
 D_B &= \overline{S(\overline{Q_A} \oplus \overline{Q_B})} + S(\overline{Q_A} \oplus \overline{Q_B}) = \overline{S \oplus \overline{Q_A} \oplus \overline{Q_B}} \\
 D_C &= \overline{S[(\overline{Q_A} \overline{Q_B}) \oplus \overline{Q_C}] + S[(\overline{Q_A} + \overline{Q_B}) \oplus \overline{Q_C}]} = \overline{[S\overline{Q_A} \overline{Q_B} + S(\overline{Q_A} + \overline{Q_B})] \oplus \overline{Q_C}} \\
 &= \overline{[S(\overline{Q_A} + \overline{Q_B}) + S(\overline{Q_A} + \overline{Q_B})] \oplus \overline{Q_C}} \\
 D_D &= \overline{S[(\overline{Q_A} \overline{Q_B} \overline{Q_C}) \oplus \overline{Q_D}] + S[(\overline{Q_A} + \overline{Q_B} + \overline{Q_C}) \oplus \overline{Q_D}]} = \overline{[S\overline{Q_A} \overline{Q_B} \overline{Q_C} + S(\overline{Q_A} + \overline{Q_B} + \overline{Q_C})] \oplus \overline{Q_D}} \\
 &= \overline{[S(\overline{Q_A} + \overline{Q_B} + \overline{Q_C}) + S(\overline{Q_A} + \overline{Q_B} + \overline{Q_C})] \oplus \overline{Q_D}} \\
 R &= \overline{S\overline{Q_A} \overline{Q_B} \overline{Q_C} \overline{Q_D}} + S\overline{Q_A} \overline{Q_B} \overline{Q_C} \overline{Q_D} \quad (\text{进位、借位输出})
 \end{aligned}$$

2.3 分频器设计：100MHz 信号通过 50,000,000 次分频后，得到 1Hz 的秒脉冲方波，作为计数器的脉冲输入。

三、实验过程和数据记录

1 实任务 1：原理图方式设计 4 位同步二进制计数器

1.1 新建工程，工程名称用 MyCounter。Top Level Source Type 用 HDL。新建源文件，类型是 Schematic。文件名称用 Counter4b。原理图方式进行设计，进行波形仿真。

设计：

```

`timescale 1ns / 1ps
module counter_4b(clk, Qa, Qb, Qc, Qd, Rc);
input wire clk;
output wire Qa, Qb, Qc, Qd, Rc;
wire Nor_nQa_nQb, Nor_nQa_nQb_nQc;

FD FD_A(.C(clk), .D(Da), .Q(Qa)),
  FD_B(.C(clk), .D(Db), .Q(Qb)),
  FD_C(.C(clk), .D(Dc), .Q(Qc)),
  FD_D(.C(clk), .D(Dd), .Q(Qd));
defparam FD_A.INIT = 1'b0, FD_B.INIT = 1'b0;
defparam FD_C.INIT = 1'b0, FD_D.INIT = 1'b0;

INV nQa_L(.I(Qa), .O(nQa)), nQb_L(.I(Qb), .O(nQb)),
  nQc_L(.I(Qc), .O(nQc)), nQd_L(.I(Qd), .O(nQd));


```

```

assign Da = nQa;

XNOR2 Db_L(.I0(Qa), .I1(nQb), .O(Db)),
Dc_L(.I0(Nor_nQa_nQb), .I1(nQc), .O(Dc)),
Dd_L(.I0(Nor_nQa_nQb_nQc), .I1(nQd), .O(Dd));
NOR4 Rc_L(.I0(nQa), .I1(nQb), .I2(nQc), .I3(nQd), .O(Rc));
NOR2 Nor_nQa_nQb_L (.I0(nQa), .I1(nQb), .O(Nor_nQa_nQb));
NOR3 Nor_nQa_nQb_nQc_L(.I0(nQa), .I1(nQb), .I2(nQc), .O(Nor_nQa_nQb_nQc
));
endmodule

```

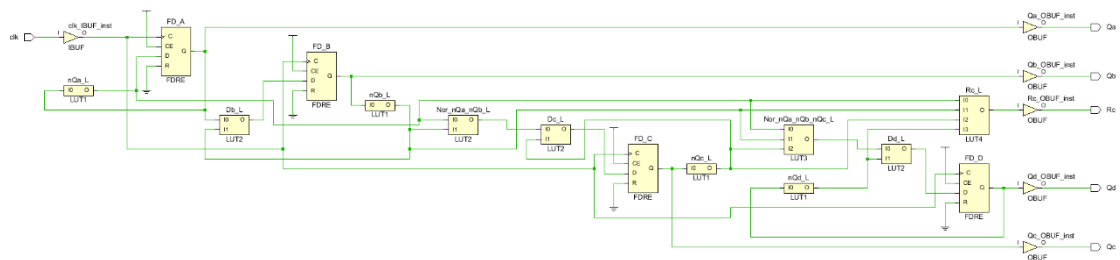


仿真:

```

`timescale 1ns / 1ps
module counter4b_test1 ();
  wire Qa, Qb, Qc, Qd, Rc;
  reg clk;
  counter_4b test1 (
    clk,
    Qa,
    Qb,
    Qc,
    Qd,
    Rc
  );
  initial
    forever begin
      clk = 1'b0;
      #100;
      clk = 1'b1;
      #100;
    end
end

```

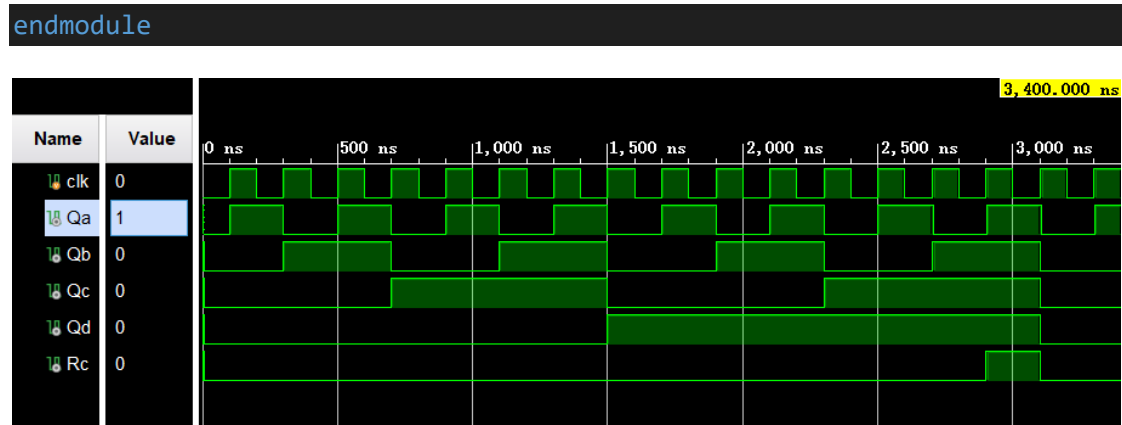

1.2 设计时钟 clk 模块

```
module clk_1s (
    clk,
    clk_1s
);
input wire clk;
output reg clk_1s;
reg [31:0] cnt;
always @(posedge clk) begin
    if (cnt < 50_000_000) begin
        cnt <= cnt + 1'b1;
    end else begin
        cnt <= 0;
        clk_1s <= ~clk_1s;
    end
end
endmodule
```


1.3 新建源文件，类型是 Verilog，文件名称用 Top。右键设为“Set as Top Module”。输入为 clk（100MHZ）时钟，每秒自增 1，显示在 1 位数码管上，Rc 显示在 LED 灯上

```
module top1 (
    clk,
    Segment,
    AN,
    Rc
);
input wire clk;
output wire [7:0] Segment;
```

```

output wire [3:0] AN;
output wire Rc;
wire[15:0] HEXS;
wire clk_1;
clk_1s d_1(clk,clk_1);
counter_4b d_2(clk_1,HEXS[0],HEXS[1],HEXS[2],HEXS[3],Rc);
DispNum d_3(clk,HEXS,4'b1110,4'b0000,0,AN,Segment);
endmodule

```

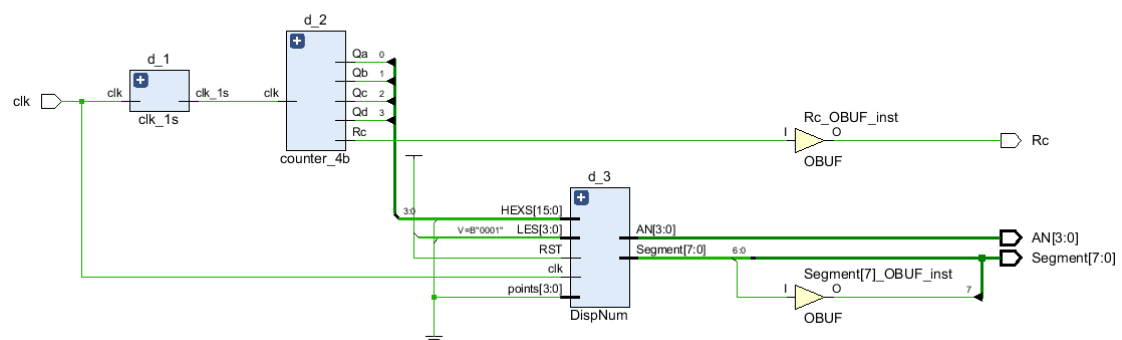

1.4 编写引脚约束文件

```

set_property PACKAGE_PIN AB22 [get_ports {Segment[0]}]
set_property PACKAGE_PIN AD24 [get_ports {Segment[1]}]
set_property PACKAGE_PIN AD23 [get_ports {Segment[2]}]
set_property PACKAGE_PIN Y21 [get_ports {Segment[3]}]
set_property PACKAGE_PIN W20 [get_ports {Segment[4]}]
set_property PACKAGE_PIN AC24 [get_ports {Segment[5]}]
set_property PACKAGE_PIN AC23 [get_ports {Segment[6]}]
set_property PACKAGE_PIN AA22 [get_ports {Segment[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[0]}]

```

```


set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]

set_property PACKAGE_PIN AC18 [get_ports clk]
set_property IOSTANDARD LVCMOS18 [get_ports clk]

set_property PACKAGE_PIN AF24 [get_ports Rc]
set_property IOSTANDARD LVCMOS33 [get_ports Rc]

```

1.5 下载至实验板，检验功能。

 

2 设计 16 位可逆同步二进制计数器

2.1 设计计数器模块，并进行仿真

设计：

```

module counter_4b_rev(clk, s, cnt, Rc);
input wire clk, s;
output reg [15:0] cnt;
output wire Rc;
initial cnt = 0;
assign Rc = (~s & (~|cnt)) | (s & (&cnt));
always @ (posedge clk) begin

```

```

    if (s)
        cnt <= cnt + 1'b1;
    else
        cnt <= cnt - 1'b1;
end
endmodule

```


仿真：

```

`timescale 1ns / 1ps
module counter_4b_rev_test1(

);
    reg clk,S;
    wire [15:0]cnt;
    wire Rc;
    integer i;
    counter_4b_rev test1(clk,S,cnt,Rc);
    initial begin
        S=0;
        for(i=0;i<18;i=i+1)begin
            clk=0;
            #50;
            clk=1;
            #50;
        end
        S=1;
        for(i=0;i<18;i=i+1)begin
            clk=0;
            #50;
            clk=1;
            #50;
        end
    end
end
endmodule

```

 

2.2 设计时钟模块


```

module clk_100ms (
    clk,
    clk_1s
);
    input wire clk;
    output reg clk_1s;
    reg [31:0] cnt;
    always @(posedge clk) begin
        if (cnt < 50_000_00) begin
            cnt <= cnt + 1'b1;
        end else begin
            cnt <= 0;
            clk_1s <= ~clk_1s;
        end
    end
end
endmodule

```


2.3 设计 top 模块

```

module top2 (
    clk,
    SW,
    Segment,
    AN,
    Rc
);
    input wire clk,SW;
    output wire [7:0] Segment;
    output wire [3:0] AN;
    output wire Rc;
    wire[15:0] HEXS;
    wire clk_1;
    clk_100ms d_1(clk,clk_1);
    counter_4b_rev d_2(clk_1,SW,HEXS[15:0],Rc);
    DispNum d_3(clk,HEXS[15:0],4'b0000,4'b0000,0,AN,Segment);
end

```

endmodule

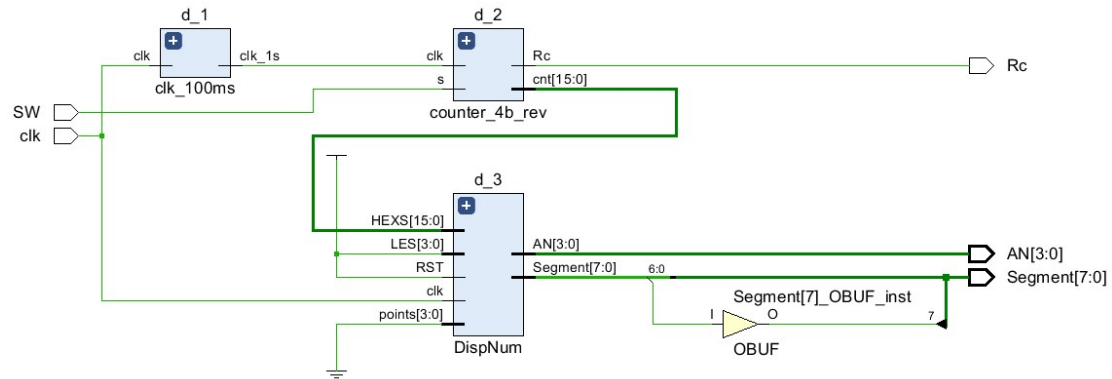

2.4 编写引脚约束文件

```
set_property PACKAGE_PIN AB22 [get_ports {Segment[0]}]
set_property PACKAGE_PIN AD24 [get_ports {Segment[1]}]
set_property PACKAGE_PIN AD23 [get_ports {Segment[2]}]
set_property PACKAGE_PIN Y21 [get_ports {Segment[3]}]
set_property PACKAGE_PIN W20 [get_ports {Segment[4]}]
set_property PACKAGE_PIN AC24 [get_ports {Segment[5]}]
set_property PACKAGE_PIN AC23 [get_ports {Segment[6]}]
set_property PACKAGE_PIN AA22 [get_ports {Segment[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[0]}]

set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]

set_property PACKAGE_PIN AC18 [get_ports clk]
```

```
set_property IOSTANDARD LVCMOS18 [get_ports clk]


set_property PACKAGE_PIN AA10 [get_ports SW]
set_property IOSTANDARD LVCMOS15 [get_ports SW]

set_property PACKAGE_PIN AF24 [get_ports Rc]
set_property IOSTANDARD LVCMOS33 [get_ports Rc]
```


2.5 下载至实验板

实验结果：

数字递增至 FFFF 亮灯：

 

数字进位递增至 0018，拨动 SW[0]，数字递减至 000d

 

四、 实验结果分析

仿真波形符合预期，数字随时间每个周期加一。

实际测验结果符合预期，实现了数字递增递减得效果。

五、 实验心得体会

调用先前模块时需注意输入参数位置，和使能是 1 还是 0。