

浙江大学

本科实验报告

课程名称：计算机逻辑设计基础

姓名：仇国智

学院：竺可桢学院

专业：计算机科学与技术

学号：3220102181

指导教师：董亚波

2023 年 10 月 16 日

一、实验目的和要求

1 目的

- 1.1 掌握变量译码器的逻辑构成和逻辑功能
- 1.2 用变量译码器实现组合函数
- 1.3 采用原理图设计电路模块
- 1.4 进一步熟悉 ISE 平台及下载实验平台物理验证

2 要求

- 2.1 原理图设计实现 74LS138 译码器模块
- 2.2 用 74LS138 译码器实现楼道灯控制，具体功能和操作同实验四任务 1


二、实验内容和原理

1 内容

- 1.1 任务 1：原理图设计实现 74LS138 译码器模块
- 1.2 任务 2：用 74LS138 译码器实现楼道灯控制器


2 原理

 - 2.1 译码器是将一种输入编码转换成另一种编码的电路，即将给定的代码进行“翻译”并转换成指定的状态或输出信号（脉冲或电平）。
- 2.2 译码可分为：变量译码、显示译码。变量译码一般是将一种较少位输入变为较多位输出的器件，如 2^n 译码和 8421BCD 码译码。显示译码主要进行 2 进制数显示成 10 进制或 16 进制数的转换，可分为驱动 LED 和 LCD 两类。
- 2.3 变量译码器是一个将 n 个输入变为 2^n 个最小项输出的多输出端的组合逻辑电路。 n 通常在 2~64 之间。




2.4 变量译码器—74LS138：带 3 个使能端的 3-8 译码器的逻辑结构由三级门电路构成，输出低电平有效。

输入			译码器输出 (低电平有效)							
使能	变量		Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
G	G_{2A}	G_{2B}	A	B	C	Y_0	Y_1	Y_2	Y_3	Y_4
\times	1	1	\times	\times	\times	1	1	1	1	1
0	\times	\times	\times	\times	\times	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1
1	0	0	0	1	0	1	0	1	1	1
1	0	0	1	0	0	1	1	0	1	1
1	0	0	1	0	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	0	1
1	0	0	1	1	1	1	1	1	0	1
1	1	0	0	0	0	1	1	1	1	0
1	1	0	0	0	1	1	1	1	1	0
1	1	0	0	1	0	1	1	1	1	0
1	1	0	0	1	1	1	1	1	1	0
1	1	1	0	0	0	1	1	1	1	0
1	1	1	0	0	1	1	1	1	1	0
1	1	1	0	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1	1	1	0

 

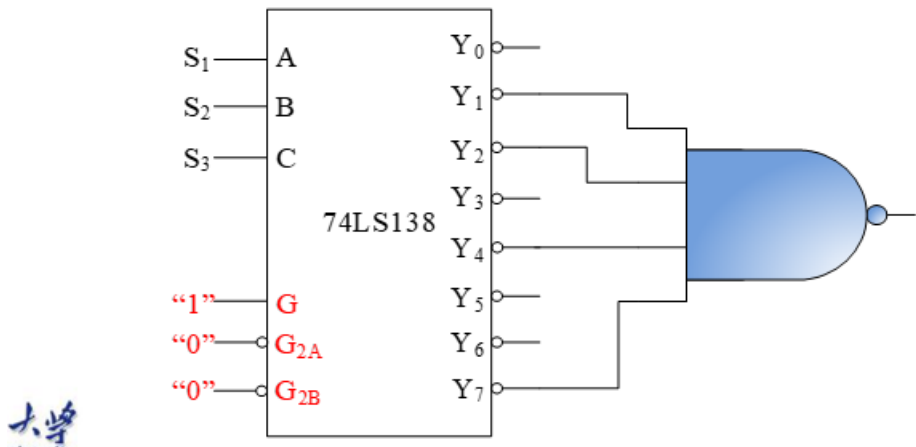2.5 变量译码器的输出对应所有输入变量的最小项组合，如果将函数转换成最小项和的形式，则可以用变量译码器实现函数的组合电路：


$$F = \overline{S_3}S_2S_1 + \overline{S_3}S_2\overline{S_1} + S_3\overline{S_2}S_1 + S_3S_2\overline{S_1}$$



三、实验过程和数据记录

1 原理图设计实现 74LS138 译码器模块

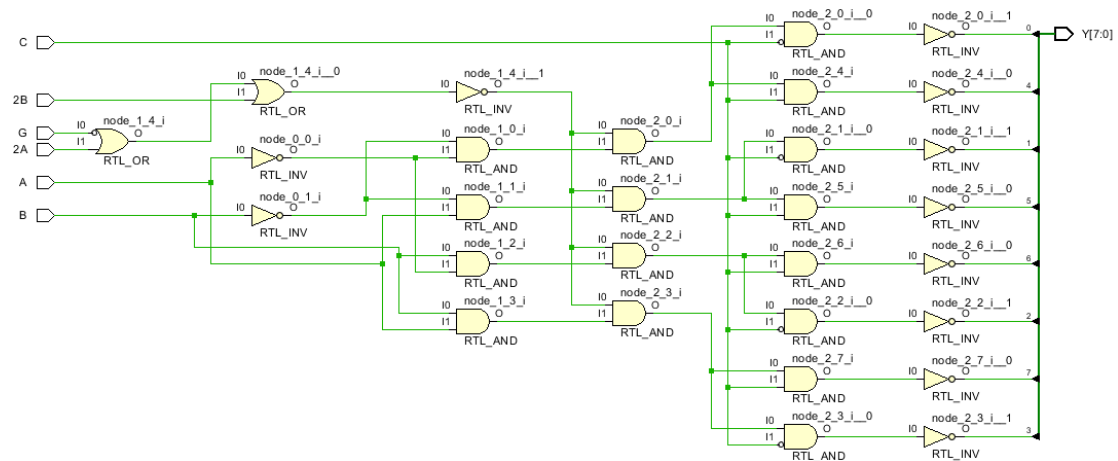1.1 新建工程，工程名称用 D_74LS138_SCH。新建 Schematic 源文件，文件名称用 D_74LS138。原理图方式进行设计。



```

`timescale 1ns / 1ps
module decoder_3_8 (
    A,
    B,
    C,
    G,
    G2A,
    G2B,
    Y
);
    input wire A, B, C, G, G2A, G2B;
    output wire [7:0] Y;
    not node_0_0 (A_n, A), node_0_1 (B_n, B), node_0_2 (C_n, C), node_0_3
(G_n, G);
    and node_1_0 (D0, B_n, A_n), node_1_1 (D1, B_n, A), node_1_2 (D2, B,
A_n), node_1_3 (D3, B, A);
    nor node_1_4 (EN, G_n, G2A, G2B);
    nand node_2_0 (
        Y[0], EN, D0, C_n
    ), node_2_1 (
        Y[1], EN, D1, C_n
    ), node_2_2 (
        Y[2], EN, D2, C_n
    ), node_2_3 (
        Y[3], EN, D3, C_n
    ), node_2_4 (
        Y[4], EN, D0, C
    ), node_2_5 (
        Y[5], EN, D1, C
    ), node_2_6 (
        Y[6], EN, D2, C
    ), node_2_7 (
        Y[7], EN, D3, C
    );
endmodule

```

```
);  
endmodule
```

1.2 Check Design Rules, 检查错误 View HDL Functional Model, 查看并学习 Verilog HDL 代码。对 D_74LS138 模块进行仿真, 激励代码如下:


```
`timescale 1ns / 1ps  
module test_tb ();  
    integer i;  
    reg A, B, C, G, G2A, G2B;  
    wire[7:0] Y;  
    decoder_3_8 UUT (  
        .A (A),  
        .B (B),  
        .C (C),  
        .G (G),  
        .G2A(G2A),  
        .G2B(G2B),  
        .Y (Y)  
    );  
    initial begin  
        A = 0;  
        B = 0;  
        C = 0;  
  
        G = 1;  
        G2A = 0;  
        G2B = 0;  
        #50;  
  
        for (i = 0; i <= 7; i = i + 1) begin  
            {C,B,A} = i;  
            #50;  
        end  
        assign G = 0;  
        assign G2A = 0;  
        assign G2B = 0;  
        #50;  
  
        assign G = 1;  
        assign G2A = 1;  
        assign G2B = 0;
```

```


#50;

assign G = 1;
assign G2A = 0;
assign G2B = 1;
#50;
end
endmodule

```

 

 - 1.3 Create Schematic Symbol, 系统生成 D_74LS138 模块的逻辑符号图文件，文件后缀.sym。符号图位于工程根目录。自动生成的符号可修改: 可以用 Tools 菜单的 Symbol Wizard, 也可以打开.sym 文件直接修改。在新工程中使用时, 把.sym 和.sch 复制到对应工程目录
- 1.4 新建工程 “D_74LS138_Test”。新建 Schematic 文件 “D_74LS138_Test”。复制 D_74LS138.sym 和.sch 到工程目录。在 symbols 框里的第一个元件, 就是 D_74LS138。用拨盘开关控制模块的输入, 用 LED(7:0)作为模块的输出, 验证模块的功能。



```

`timescale 1ns / 1ps

```

```

module test(S1,
    S2,
    S3,
    S4,
    S5,
    S6,
    LED);
    input wire S1,S2,S3,S4,S5,S6;
    output wire [7:0] LED;
    decoder_3_8(S1,S2,S3,S4,S6,S5,LED);
endmodule

```

1.5 建立引脚文件，下载验证，根据真值表，操作实验板，验证功能。


```

set_property IOSTANDARD LVCMOS33 [get_ports {LED[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[0]}]
set_property PACKAGE_PIN W23 [get_ports {LED[0]}]
set_property PACKAGE_PIN AB26 [get_ports {LED[1]}]
set_property PACKAGE_PIN Y25 [get_ports {LED[2]}]
set_property PACKAGE_PIN AA23 [get_ports {LED[3]}]
set_property PACKAGE_PIN Y23 [get_ports {LED[4]}]
set_property PACKAGE_PIN Y22 [get_ports {LED[5]}]
set_property PACKAGE_PIN AE21 [get_ports {LED[6]}]
set_property PACKAGE_PIN AF24 [get_ports {LED[7]}]
set_property IOSTANDARD LVCMOS15 [get_ports S1]
set_property IOSTANDARD LVCMOS15 [get_ports S2]
set_property IOSTANDARD LVCMOS15 [get_ports S3]
set_property PACKAGE_PIN AA10 [get_ports S1]
set_property PACKAGE_PIN AB10 [get_ports S2]
set_property PACKAGE_PIN AA13 [get_ports S3]
#set_property PACKAGE_PIN AF24 [get_ports F]
#set_property IOSTANDARD LVCMOS33 [get_ports F]
set_property IOSTANDARD LVCMOS15 [get_ports S4]
set_property IOSTANDARD LVCMOS15 [get_ports S5]
set_property IOSTANDARD LVCMOS15 [get_ports S6]
set_property PACKAGE_PIN AA12 [get_ports S4]
set_property PACKAGE_PIN Y13 [get_ports S5]

```

```
set_property PACKAGE_PIN Y12 [get_ports S6]
```

Name	Direction	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type	Pull Type
All ports (14)											
LED (8)											
LE...	OUT		AF24	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		AE21	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		Y22	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		Y23	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		AA23	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		Y25	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		AB26	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
LE...	OUT		W23	✓	12	LVC MOS33*	3.300		12	SLOW	NONE
Scalar ports (6)											
S1	IN		AA10	✓	33	LVC MOS15*	1.500				NONE
S2	IN		AB10	✓	33	LVC MOS15*	1.500				NONE
S3	IN		AA13	✓	33	LVC MOS15*	1.500				NONE
S4	IN		AA12	✓	33	LVC MOS15*	1.500				NONE
S5	IN		Y13	✓	33	LVC MOS15*	1.500				NONE
S6	IN		Y12	✓	33	LVC MOS15*	1.500				NONE

 

2 用 74LS138 译码器实现楼道灯控制器

2.1 新建工程 LampCtrl138。复制 D_74LS138.sym 和.sch 文件到工程目录。在 symbols 框里的第一个元件,就是 D_74LS138。根据前面原理,用原理图方式输入。1 用 VCC, 0 用 GND。


```
`timescale 1ns / 1ps
module LampCtrl (
    S1,
    S2,
    S3,
    F
);
    input wire S1, S2, S3;
    output wire F;
    wire[7:0] out;
    wire G,G2A,G2B;
    VCC vcc1(G);
```



```

GND gnd1(G2A), gnd2(G2B);
decoder_3_8 gate1(S1,S2,S3,G,G2A,G2B,out);
nand gate2s(F,out[1],out[2],out[4],out[7]);
endmodule

```

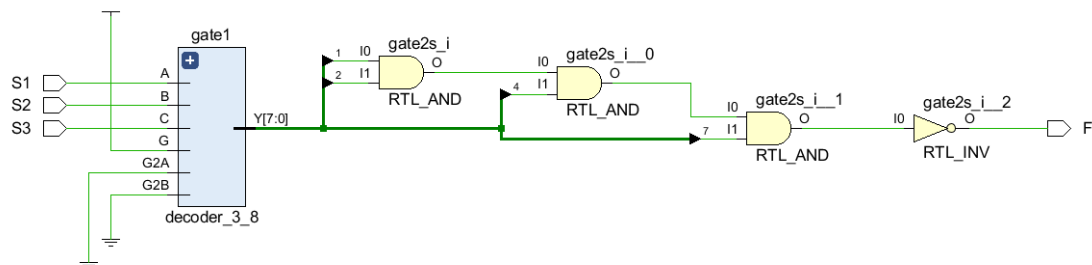

2.2 建立基准测试波形文件，输出仿真波形图。

```

`timescale 1ns / 1ps
module tb_lampctrl_1 ();
    // Inputs
    reg S1;
    reg S2;
    reg S3;

    // Output
    wire F;

    // Bidirs

    // Instantiate the UUT
    LampCtrl UUT1 (
        .S1(S1),
        .S2(S2),
        .S3(S3),
        .F (F)
    );

    // Initialize Inputs
    // `ifdef auto_init
    initial begin
        S1 = 0;
        S2 = 0;
        S3 = 0;
        #50 S1 = 1;
        #50 S1 = 0;
    end


```

```

    S2 = 1;
    #50 S1 = 1;
    #50 S1 = 0;
    S2 = 0;
    S3 = 1;
    #50 S1 = 1;
    #50 S1 = 0;
    S2 = 1;
    #50 S1 = 1;
    #50 S1 = 0;
    S2 = 0;
    S3 = 0;
end
// `endif

endmodule

```

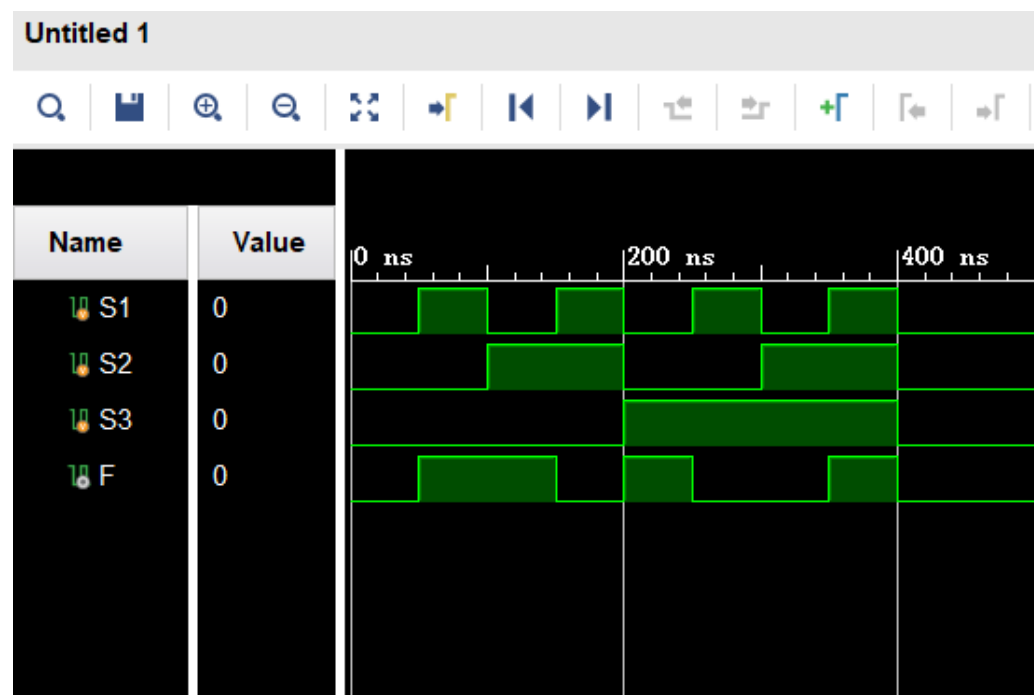

```

`timescale 1ns / 1ps
module tb_lampctrl_2 ();
    // Inputs
    reg S1;
    reg S2;
    reg S3;
    // Output

```

```

wire F;

// Bidirs

// Instantiate the UUT
LampCtrl UUT2 (
    .S1(S1),
    .S2(S2),
    .S3(S3),
    .F (F)
);
// Initialize Inputs
// `ifdef auto_init
integer i;
initial begin
    for (i = 0; i <= 8; i = i + 1) begin
        {S3, S2, S1} <= i;
        #50;
    end
end
// `endif

endmodule


```



2.3 在 ucf 文件里输入必要的引脚约束。下载验证，使用 SW[1]-SW[3]控制 1 个 LED 开关。

```
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[7]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[6]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[5]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[4]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[3]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[2]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[1]}]
# set_property IOSTANDARD LVCMOS33 [get_ports {LED[0]}]
# set_property PACKAGE_PIN W23 [get_ports {LED[0]}]
# set_property PACKAGE_PIN AB26 [get_ports {LED[1]}]
# set_property PACKAGE_PIN Y25 [get_ports {LED[2]}]
# set_property PACKAGE_PIN AA23 [get_ports {LED[3]}]
# set_property PACKAGE_PIN Y23 [get_ports {LED[4]}]
# set_property PACKAGE_PIN Y22 [get_ports {LED[5]}]
# set_property PACKAGE_PIN AE21 [get_ports {LED[6]}]
# set_property PACKAGE_PIN AF24 [get_ports {LED[7]}]
set_property IOSTANDARD LVCMOS15 [get_ports S1]
set_property IOSTANDARD LVCMOS15 [get_ports S2]
set_property IOSTANDARD LVCMOS15 [get_ports S3]
set_property PACKAGE_PIN AA10 [get_ports S1]
set_property PACKAGE_PIN AB10 [get_ports S2]
set_property PACKAGE_PIN AA13 [get_ports S3]
set_property PACKAGE_PIN AF24 [get_ports F]
set_property IOSTANDARD LVCMOS33 [get_ports F]
# set_property IOSTANDARD LVCMOS15 [get_ports S4]
# set_property IOSTANDARD LVCMOS15 [get_ports S5]
# set_property IOSTANDARD LVCMOS15 [get_ports S6]
# set_property PACKAGE_PIN AA12 [get_ports S4]
# set_property PACKAGE_PIN Y13 [get_ports S5]
# set_property PACKAGE_PIN Y12 [get_ports S6]
```

I/O Ports x												
Name	Direction	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type	Pull Type	Off-Chip Termination
All ports (4)												
Scalar ports (4)												
OUT			AF24	<input checked="" type="checkbox"/>	12	...	3.300	12	SLOW	NONE	FP_VTT_50	
IN			AA10	<input checked="" type="checkbox"/>	33	...	1.500			NONE	NONE	
IN			AB10	<input checked="" type="checkbox"/>	33	...	1.500			NONE	NONE	
IN			AA13	<input checked="" type="checkbox"/>	33	...	1.500			NONE	NONE	

 

四、实验结果分析

仿真波形与 ppt 一致，任务一下载验证时，按二进制码的顺序拨动 SW 开关，显示灯依次熄灭，任务二下载验证时，只有当奇数个开关开启时，显示灯才亮。

五、讨论心得

我们每一个文件都相当于是一个元器件，括号里面的内容为此元器件的输入输出接口。对于 top module 来说，接口用于在引脚约束以后，对应于开发板上一个个按钮、LED 灯等 器件，供我们在开发板上手动操作并观察效果。对于其他元器件来说，接口就是供被调用使用的。