洲江水学

本科实验报告

课程名称:	计算机逻辑设计基础			
姓 名:	仇国智			
学 院:	竺可桢学院			
专 业:	计算机科学与技术			
学 号:	3220102181			
指导教师:	董亚波			

2023年10月28日


一、实验目的和要求

- 1 实验目的
 - 1.1 掌握数据选择器的工作原理和逻辑功能
 - 1.2 掌握数据选择器的使用方法
 - 1.3 掌握 4 位数码管扫描显示方法
 - 1.4 4位数码管显示应用一记分板设计台
- 2 实验任务
 - 2.1 任务 1: 数据选择器设计
- 2.2 任务 2: 记分板设计
- 二、实验内容和原理
- 1 实验内容
 - 1.1 数据选择器设计
 - 1.2 记分板设计: 子任务 1: 实现 4 位 7 段数码管动态扫描显示; 子任务 2: 实现计分板功能。用 BTNX4Y3~BTNX4Y0 这 4 个按钮从左向右分别控制 4 位数码管,每个按钮按一次,对 应数码管加 1。


2 实验原理

2.1 选一多路选择器: MUX4to1: 根据事件简化真值表。输出是 控制信号全部最小项与或结构。


信息输入	控制端		选择输出			
I0 I1 I2 I3	S1	S0	0		输出	项
I0 I1 I2 I3	0	0	10	1	S1S0	Ι0
I0 I1 I2 I3	0	1	I1		<u></u> S1S0	I1
I0 I1 I2 I3	1	0	12		S1S0	I2
I0 I1 I2 I3	1	1	I3	Į	<u>\$150</u>	I3

 

2.2 控制结构不变,每路输入向量化

 

 2.3 动态扫描显示方案:扫描信号来自时钟计数分频器:时序转化为组合电路。由板载时钟 clk(100MHz)作为计数器时钟,分频后的高两位信号(clk_div[18:17])作为扫描控制信号Scan[1:0],其数据为从0、1、2、3、0、……,输入2-4译码器产生数码管位选信号,控制哪个数码管显示(位选择),同时输入4选1多路复用器选择需要显示哪个数据(段码选择)计数器的分频系数要适当,几 ms 切换一次。




三、实验过程和数据记录


- 1 数据选择器设计
- 1.1 原理图方式设计 1 位和 4 位 4 选 1 数据选择器

```
`timescale 1ns / 1ps
module Mux4to14b (
    S,
    I0,
    I1,
    I2,
    I3,
     0
);
    input wire [1:0] S;
    input wire [3:0] I0, I1, I2, I3;
    output wire [3:0] O;
    wire S00, S01, S10, S11;
    wire [3:0] i0, i1, i2, i3;
```

```
assign i0[3:0] = ~I0[3:0], i1[3:0] = ~I1[3:0], i2[3:0] = ~I2[3:0],
i3[3:0] = ~I3[3:0];
assign S00 = !S[1] & !S[0], S01 = !S[1] & S[0], S10 = S[1] & !S[0],
S11 = S[0] & S[1];
assign O[0] = S00 & i0[0] | S00 & i1[0] | S00 & i2[0] | S00 & i3[0];
assign O[1] = S01 & i0[1] | S01 & i1[1] | S01 & i2[1] | S01 & i3[1];
assign O[2] = S10 & i0[2] | S10 & i1[2] | S10 & i2[2] | S10 & i3[2];
assign O[3] = S11 & i0[3] | S11 & i1[3] | S11 & i2[3] | S11 & i3[3];
endmodule
```

 


```
module Mux4to1 (
    S,
    I0,
    I1,
    I2,
    I3,
    O
);
    input wire [1:0] S;
    input wire I0, I1, I2, I3;
    output wire 0;
    wire S00, S01, S10, S11;
    assign S00 = !S[1] & !S[0], S01 = !S[1] & S[0], S10 = S[1] & !S[0],
S11 = S[0] & S[1];
    assign 0 = S00 & I0 | S01 & I1 | S10 & I2 | S11 & I3;
endmodule
```

 

 
1.2 建立仿真波形文件, 初始化 I0、I1、I2、I3 和 S[1:0], 进行仿真 Mux4to14b:

```
timescale 1ns / 1ps
module test1 ();
  integer i;
 reg [1:0] S;
  reg [3:0] I0, I1, I2, I3;
  wire [3:0] 0;
 Mux4to14b test1 (
      S,
     Ι0,
     I1,
     Ι2,
     Ι3,
      0
  );
  initial begin
   I0 = 4'b0001;
   I1 = 4'b0010;
   I2 = 4'b0100;
   I3 = 4'b1000;
   for (i = 0; i < 4; i = i + 1) begin
     S = i;
     #200;
```



Mux4to1:
 
```
`timescale 1ns / 1ps
module test2 ();
 integer i;
 reg [1:0] S;
 reg I0, I1, I2, I3;
 wire 0;
 Mux4to1 test2 (
     S,
     Ι0,
     Ι1,
     I2,
     Ι3,
     0
  );
 initial begin
   I0 = 1'b1;
   I1 = 1'b0;
   I2 = 1'b0;
   I3 = 1'b0;
   for (i = 0; i < 4; i = i + 1) begin
    S = i;
     #200;
     {I3,I2,I1,I0}=2*{I3,I2,I1,I0};
```



1.3

- 2 记分板设计
 - 2.1 用原理图形式设计 DisplaySync 模块

输入:

Hexs(15:0): 需要显示的 4 个 4 位二进制数

point(3:0): 每位数码管的小数点

LES(3:0): 每位数码管是否需要消隐

Scan(1:0): 扫描控制信号

输出:


HEX(3:0): 当前要显示的 4 位二进制数

AN(3:0): 4位数码管的位选择信号(低电平有效)

P、LE: 小数点和消隐控制

```
module dispsync (
   input [15:0] Hexs,
   input [1:0] Scan,
   input [3:0] Point,
   input [3:0] Les,
   output reg [3:0] Hex,
   output reg p,
   output reg LE,
   output reg [3:0] AN
 always @* begin
   case (Scan)
     2'b00: begin
       Hex <= Hexs[3:0];</pre>
       AN <= 4'b1110;
       p <= Point[0];</pre>
       LE <= Les[0];
```
 
```
2'b01: begin
    Hex <= Hexs[7:4];</pre>
    AN <= 4'b1101;
        <= Point[1];
    LE <= Les[1];
  2'b10: begin
    Hex <= Hexs[11:8];</pre>
    AN <= 4'b1011;
        <= Point[2];
    р
    LE <= Les[2];
  2'b11: begin
    Hex <= Hexs[15:12];</pre>
    AN <= 4'b0111;
        <= Point[3];
    LE <= Les[3];
endcase
```



2.2 设计 32 位时钟计数分频器输入:

clk: 实验板主时钟

rst: 复位信号


输出:

clkdiv(31:0): 分频时钟输出

```
module clkdiv (
    input clk,
    input rst,
    output reg [31:0] clkdiv
);
    always @(posedge clk or posedge rst) begin
    if (rst) clkdiv <= 0;
    else clkdiv <= clkdiv + 1'b1;
    end
endmodule</pre>
```

 2.3 设计实现 4 位 7 段数码管动态扫描显示 DispNum 模块

```
`timescale 1ns / 1ps
module DispNum(
clk,
HEXS,
LES,
points,
RST,
AN,
Segment
    );
    input wire clk,RST;
    input wire[3:0]LES,points;
   output wire[3:0]AN;
   input wire[15:0] HEXS;
   output wire[7:0] Segment;
   wire[31:0]clkd;
   wire [3:0]HEX;
   wire point,LE;
    clkdiv d0(clk,RST,clkd);
   dispsync d1(HEXS,clkd[18:17],points,LES,HEX,point,LE,AN);
    MvMC14495
d2(HEX[0],HEX[1],HEX[2],HEX[3],point,LE,Segment[0],Segment[1],Segment[2
],Segment[3],Segment[4],Segment[5],Segment[6],Segment[7]);
endmodule
```




2.4 设计 CreateNumber 按键数据输入模块。使用行为描述设计: 四个按键,各按一下,4个4位2进制数分别加1。

```
module CreateNumber (
    input wire [ 3:0] btn,
    output reg [15:0] num
);
    wire [3:0] A, B, C, D;
    initial num <= 16'b1010_1011_1100_1101;
    assign A = num[3:0] + 4'd1;
    assign B = num[7:4] + 4'd1;
    assign C = num[11:8] + 4'd1;
    assign D = num[15:12] + 4'd1;
    always @(posedge btn[0]) num[3:0] <= A;
    always @(posedge btn[1]) num[7:4] <= B;
    always @(posedge btn[2]) num[11:8] <= C;
    always @(posedge btn[3]) num[15:12] <= D;
endmodule</pre>
```

 2.5 新建源文件 top, 在右键菜单里设为"Top Module"

```
module top (
    input wire clk,
    input wire [7:0] SW,
    input wire [3:0] btn,
    output wire [3:0] AN,
    output wire [7:0] SEGMENT,
    output wire BTNX4
);
    wire [15:0] num;
    wire gnd;
```

```
CreateNumber c0 (
    btn,
    num
);
assign BTNX4=1'b0;
DispNum d0 (
    clk,
    num,
    SW[7:4],
    SW[3:0],
    1'b0,
    AN,
    SEGMENT
);
endmodule
```



2.6 编写引脚约束文件

```
set_property PACKAGE_PIN W14 [get_ports {btn[0]}]
set_property PACKAGE_PIN V14 [get_ports {btn[1]}]
set_property PACKAGE_PIN V19 [get_ports {btn[2]}]
set_property PACKAGE_PIN V18 [get_ports {btn[3]}]
set_property PACKAGE_PIN W16 [get_ports BTNX4]
set_property PACKAGE_PIN AC18 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[7]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SEGMENT[0]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[7]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[6]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[5]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[4]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[3]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[2]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[1]}]
set_property IOSTANDARD LVCMOS15 [get_ports {SW[0]}]
set_property PACKAGE_PIN AA10 [get_ports {SW[0]}]
set_property PACKAGE_PIN AB10 [get_ports {SW[1]}]
set_property PACKAGE_PIN AA13 [get_ports {SW[2]}]
set_property PACKAGE_PIN AA12 [get_ports {SW[3]}]
set_property PACKAGE_PIN Y13 [get_ports {SW[4]}]
set_property PACKAGE_PIN Y12 [get_ports {SW[5]}]
set_property PACKAGE_PIN AD11 [get_ports {SW[6]}]
set_property PACKAGE_PIN AD10 [get_ports {SW[7]}]
set_property PACKAGE_PIN AB22 [get_ports {SEGMENT[0]}]
set_property PACKAGE_PIN AD24 [get_ports {SEGMENT[1]}]
set_property PACKAGE_PIN AD23 [get_ports {SEGMENT[2]}]
set_property PACKAGE_PIN Y21 [get_ports {SEGMENT[3]}]
set_property PACKAGE_PIN W20 [get_ports {SEGMENT[4]}]
set_property PACKAGE_PIN AC24 [get_ports {SEGMENT[5]}]
set_property PACKAGE_PIN AC23 [get_ports {SEGMENT[6]}]
set_property PACKAGE_PIN AA22 [get_ports {SEGMENT[7]}]
set_property PACKAGE_PIN AD21 [get_ports {AN[0]}]
set_property PACKAGE_PIN AC21 [get_ports {AN[1]}]
set_property PACKAGE_PIN AB21 [get_ports {AN[2]}]
set_property PACKAGE_PIN AC22 [get_ports {AN[3]}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {btn[0]}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {btn[1]}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {btn[2]}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {btn[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports {btn[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports {btn[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports {btn[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports {btn[0]}]
```

set_property IOSTANDARD LVCMOS18 [get_ports BTNX4] set_property IOSTANDARD LVCMOS18 [get_ports clk]



2.7 生成并下载 bit 文件,进行实际测试测试小数点控制:



测试数字消隐:



测试按键数字递增:









四、实验结果分析

波形图同 ppt 相同,输出随 O 随选择信号线 S 在 I0,I1,I2,I3 中依次选择输出;下载验证符合预期,小数点随开关拨动依次亮起,数字随开关拨动依次消隐,每按一次键数字会发生变化。但是唯一的不足是数字每次不是只变化 1。

五、讨论与心得

按钮按下过程中电压不稳定,会导致数字递增多次,可以使用开关来 稳定,或者采用其它方式避免电压波动造成的影响。